
# **RISC-V Design**

# A non-pipelined RISC architecture

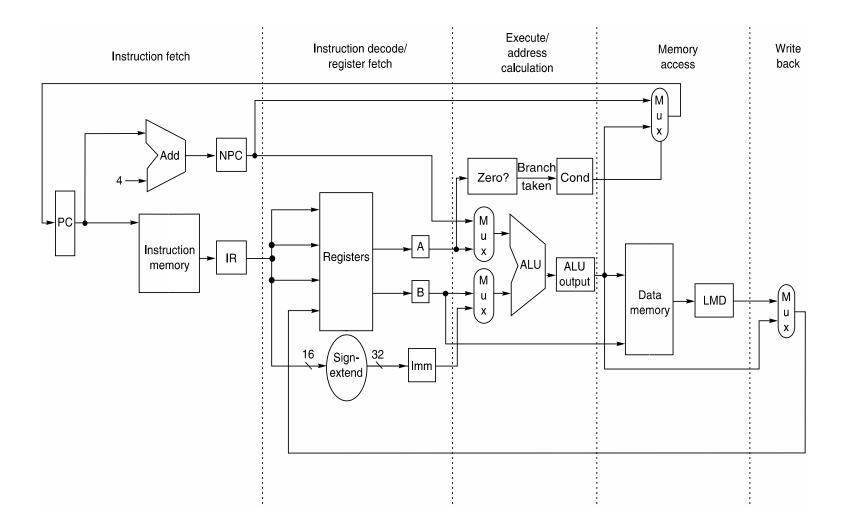

# **Opcodes**

- Defines the "opcode" for various classes of operations
- ▶ For 32-bit instruction words, the 2 LSBs are always 11

inst[4:2] inst[6:5]	000	001	010	011	100	101	110	111
00	LOAD	LOAD-FP	custom-0	MISC-MEM	OP-IMM	AUIPC	OP-IMM-32	48b
01	STORE	STORE-FP	custom-1	AMO	OP	LUI	OP-32	64b
10	MADD	MSUB	NMSUB	NMADD	OP-FP	reserved	custom-2/rv128	48b
11	BRANCH	JALR	reserved	JAL	SYSTEM	reserved	custom-3/rv128	>= 80b

LUI		imm[31:12]	rd	0110111		
AUIPC		imm[31:12]			rd	0010111
JAL	i	mm[20 10:1 11 19	9:12]		rd	1101111
JALR	imm[11:0	)]	rs1	000	rd	1100111
BEQ	imm[12 10:5]	rs2	rs1	000	imm[4:1 11]	1100011
BNE	imm[12 10:5]	rs2	rs1	001	imm[4:1 11]	1100011
BLT	imm[12 10:5]	rs2	rs1	100	imm[4:1 11]	1100011
BGE	imm[12 10:5]	rs2	rs1	101	imm[4:1 11]	1100011
BLTU	imm[12 10:5]	rs2	rs1	110	imm[4:1 11]	1100011
BGEU	imm[12 10:5]	rs2	rs1	111	imm[4:1 11]	1100011
LB	imm[11:0	rs1	000	rd	0000011	
LH	imm[11:0	rs1	001	rd	0000011	
LW	imm[11:0	rs1	010	rd	0000011	
LBU	imm[11:0	rs1	100	rd	0000011	
LHU	imm[11:0	)]	rs1	101	rd	0000011
SB	imm[11:5]	rs2	rs1	000	imm[4:0]	0100011
SH	imm[11:5]	rs2	rs1	001	imm[4:0]	0100011
SW	imm[11:5]	rs2	rs1	010	imm[4:0]	0100011
ADDI	imm[11:0	-	rs1	000	rd	0010011
SLTI	imm[11:0	)]	rs1	010	rd	0010011
SLTIU	imm[11:0	)]	rs1	011	rd	0010011
XORI	imm[11:0	)]	rs1	100	rd	0010011
ORI	imm[11:0	)]	rs1	110	rd	0010011
ANDI	imm[11:0	)]	rs1	111	rd	0010011
SLLI	0000000	shamt	rs1	001	rd	0010011
SRLI	0000000	shamt	rs1	101	rd	0010011
SRAI	0100000	shamt	rs1	101	rd	0010011
ADD	0000000	rs2	rs1	000	rd	0110011
SUB	0100000	rs2	rs1	000	rd	0110011
SLL	0000000	rs2	rs1	001	rd	0110011
SLT	0000000	rs2	rs1	010	rd	0110011
SLTU	0000000	rs2	rs1	011	rd	0110011
XOR	0000000	rs2	rs1	100	rd	0110011
SRL	0000000	rs2	rs1	101	rd	0110011
SRA	0100000	rs2	rs1	101	rd	0110011
OR	0000000	rs2	rs1	110	rd	0110011
AND	0000000	rs2	rs1	111	rd	0110011


**U-type** U-type J-type I-type **B-type** B-type B-type B-type **B-type** B-type I-type I-type I-type I-type I-type S-type S-type S-type I-type I-type I-type I-type I-type I-type R-type R-type

funct7	rs2	rs1	funct3	rd	opcode
imm[11:	0]	rs1	funct3	rd	opcode
imm[11:5]	rs2	rs1	funct3	imm[4:0]	opcode
imm[12 10:5]	rs2	rs1	funct3	imm[4:1 11]	opcode
	imm[31:12]		rd	opcode	
ir	nm[20 10:1 11 1		rd	opcode	
	İ	! ! !			

R-type I-type S-type B-type U-type J-type

JAL	ir	nm[20 10:1 11 1	9:12]		rd	1101111
BEQ	imm[12 10:5]	rs2	rs1	000	imm[4:1 11]	1100011
BNE	imm[12 10:5]	rs2	rs1	001	imm[4:1 11]	1100011
BLT	imm[12 10:5]	rs2	rs1	100	imm[4:1 11]	1100011
BGE	imm[12 10:5]	rs2	rs1	101	imm[4:1 11]	1100011
LW	imm[11:0	rs1	010	rd	0000011	
SW	imm[11:5]	rs2	rs1	010	imm[4:0]	0100011
ADDI	imm[11:0	rs1	000	rd	0010011	
XORI	imm[11:0	rs1	100	rd	0010011	
ORI	imm[11:0	rs1	110	rd	0010011	
ANDI	imm[11:0	rs1	111	rd	0010011	
ADD	0000000	rs2	rs1	000	rd	0110011
SUB	0100000	rs2	rs1	000	rd	0110011
XOR	0000000	rs2	rs1	100	rd	0110011
OR	0000000	rs2	rs1	110	rd	0110011
AND	0000000	rs2	rs1	111	rd	0110011

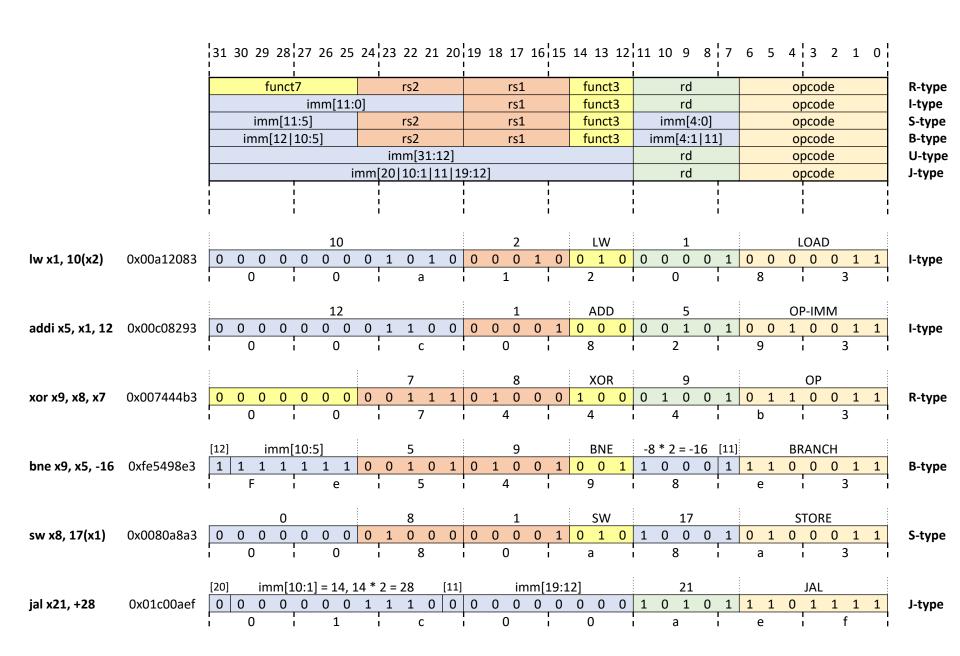J-type **B-type B-type B-type B-type** I-type S-type I-type I-type I-type I-type R-type R-type R-type R-type R-type



#### **RISC-V** online resources


#### Online RISC-V assembler

- https://riscvasm.lucasteske.dev/#
- Make sure you select only RV32I instructions!

#### Online RISC-V C compiler

- https://godbolt.org/
- Select the C language
- Select a RISC-V compiler (per esempio gcc) for the 32-bit architecture
- Unfortunately we can't constrain the compiler to generate code for the base ISA only (it might include instructions that you have not implemented!)

# **RISC-V** online compiler

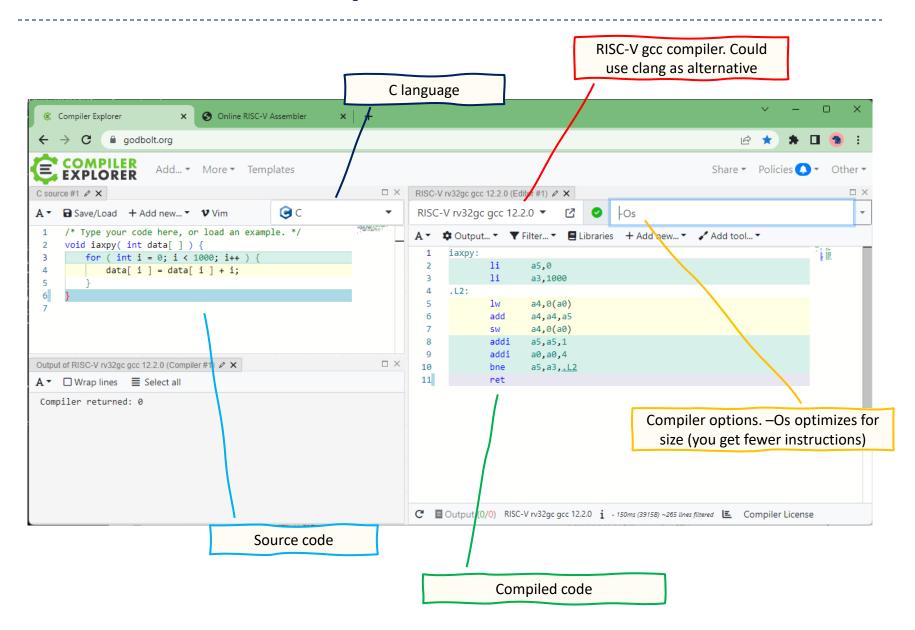

**RISC-V** online assembler Compiler Explorer Online RISC-V Assembler → G in riscvasm.lucasteske.dev/# \* 🗆 😘 **RISC-V Online Assembler** Copy code here Type the assembly code below and click Build a5,0 a3,1000 a4,0(a0) a4,a4,a5 a5,a5,1 a0,a0,4 a5,a3,.L2 Hit "BUILD" ret BUILD Get the hex dump to be copied in **Hex Dump** instruction memory initialization fed796e3 Also get the hex to code correspondence

## **Example**

```
void iaxpy( int data[ ] ) {
    for ( int i = 0; i < 1000; i++ ) {
        data[ i ] = data[ i ] + 1;
    }
}</pre>
```

Program							
		0		0	ADDI	15	OP-IMM
li a5,0	0x00000793	0 0 0 0 0 0 0 0	0 0 0 0	0 0 0 0	0 0 0	0 1 1 1 1	0 0 1 0 0 1 1
		1000		0	ADDI	13	OP-IMM
li a3,1000	0x3e800693	0 0 1 1 1 1 1 0	1 0 0 0	0 0 0 0	0 0 0	0 1 1 0 1	0 0 1 0 0 1 1
loop:		0		10	LW	14	LOAD
lw a4,0(a0)	0x00052703	0 0 0 0 0 0 0	0 0 0 0	0 1 0 1 0	0 1 0	0 1 1 1 0	0 0 0 0 0 1 1
		0	15	14	ADD	14	OP
add a4,a4,a5	0x00f70733	0 0 0 0 0 0 0 0	1 1 1 1	0 1 1 1 0	0 0 0	0 1 1 1 0	0 1 1 0 0 1 1
		0	14	10	SW	0	STORE
sw a4,0(a0)	0x00e52023	0 0 0 0 0 0 0 0	1 1 1 0	0 1 0 1 0	0 1 0	0 0 0 0	0 1 0 0 0 1 1
		1		15	ADDI	15	OP-IMM
addi a5,a5,1	0x00178793						
	0.0001.0750	0 0 0 0 0 0 0	0 0 0 1	0 1 1 1 1	0 0 0	0 1 1 1 1	0 0 1 0 0 1 1
	0.001,0,00	4	0 0 0 1	0 1 1 1 1	0 0 0 ADDI	0 1 1 1 1	0 0 1 0 0 1 1 OP-IMM
addi a0,a0,4	0x00450513	4	0 0 0 1				· · · · · · · · · · · · · · · · · · ·
addi a0,a0,4		4		10	ADDI	10	OP-IMM
addi a0,a0,4 bne a5,a3,loop	0x00450513	4 0 0 0 0 0 0 0 0 0 negative	0 1 0 0	10 0 1 0 1 0	ADDI 0 0	10 0 1 0 1 0	OP-IMM 0 0 1 0 0 1 1

#### Notes:

- Registers a0, a1, a2, etc. correspond to x10, x11, x12, etc. (it is a standard naming convention)
- **a0** is the pointer to the array in memory (initially zero?)
- a5 contains the current loop index (variable i in the C code)
- a3 is the end of loop condition (1000)
- **a4** is a temporary that holds the value loaded from memory (data[i]), then it gets added to **a5** (the index) and is stored back to memory (data[i])
- Branch checks if the index (a5) has not reached the end (a3)

# **Example architecture**

#### **Instruction Fetch**


#### Instruction Memory

- Defined as 1024 words of 32 bits each, total of 4 kB
  - Address is 10 bits
- Using a BRAM, it has an output register
  - Instruction code available only in the clock cycle that follows the new value of the program counter
- Could be potentially be placed outside, to be more general

#### Program Counter (PC)

- Must address 4 kB, hence it is 12 bits if addressing bytes
  - ▶ The two least significant bits will always be 0, removed when connecting to instruction memory
  - PC arithmetic in the ALU done at byte level
- ▶ The stage computes the address of the next instruction, by adding 4 for the PC
- Load enable (pc\_load) activated by control state machine

### **Instruction fetch**

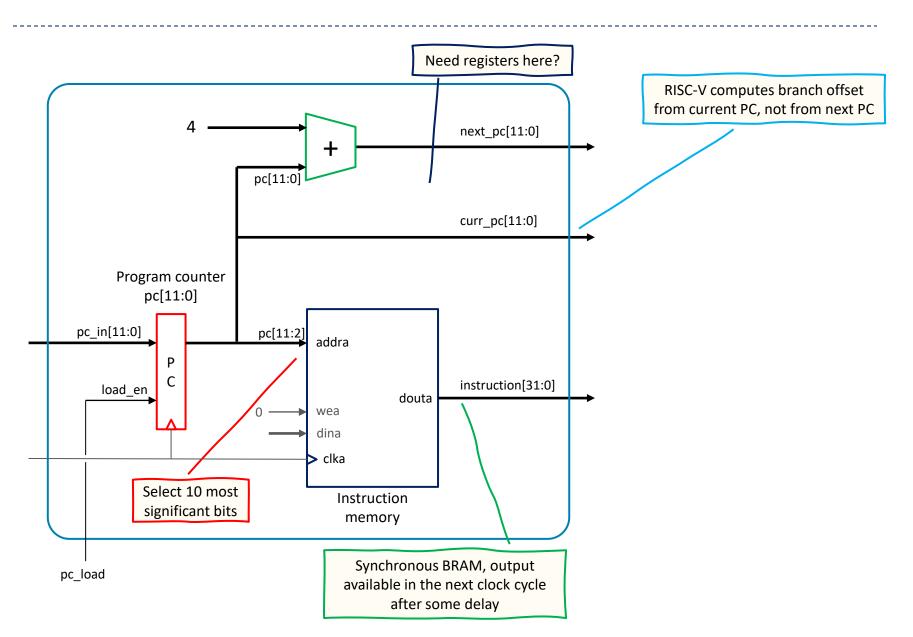

#### **Instruction Decode**


#### Register file

- Defined as 32 words of 32 bits each, two ports, distributed memory
  - First port used to read and write, at different times
  - Address (source or destination) chosen depending on instruction execution phase
  - write\_en generated by control state machine
  - Latched output, since we would need to add it anyway

#### Decoding logic and sign extension

- Checks instruction class and defines operand selection signals
- Defines operation signal for ALU and comparator
- Selects immediate fields and reconstructs the sign extended immediate according to the instruction class
- Outputs are latched

#### Instruction decode

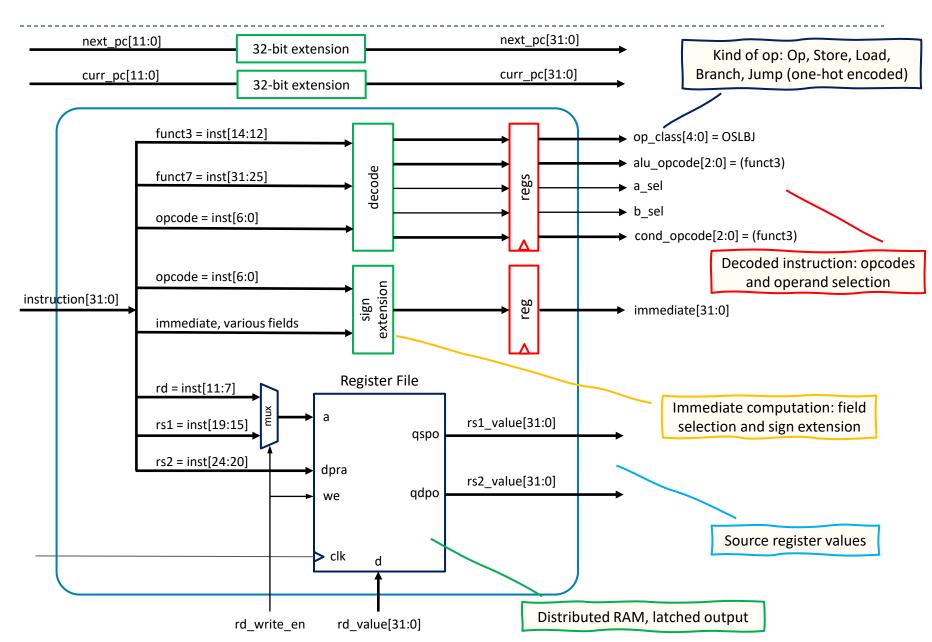

#### **Instruction Execute**


#### ALU

- Implements a subset of arithmetic and logic operations
- Muxes at inputs select the operands
- Opcode generally follows the RISC-V standard convention
- ▶ Both latched and unlatched outputs available

#### Comparator

- Used for branch operations, compares register values according to opcode
- Output determines if branch is to be taken or not

#### Instruction execute

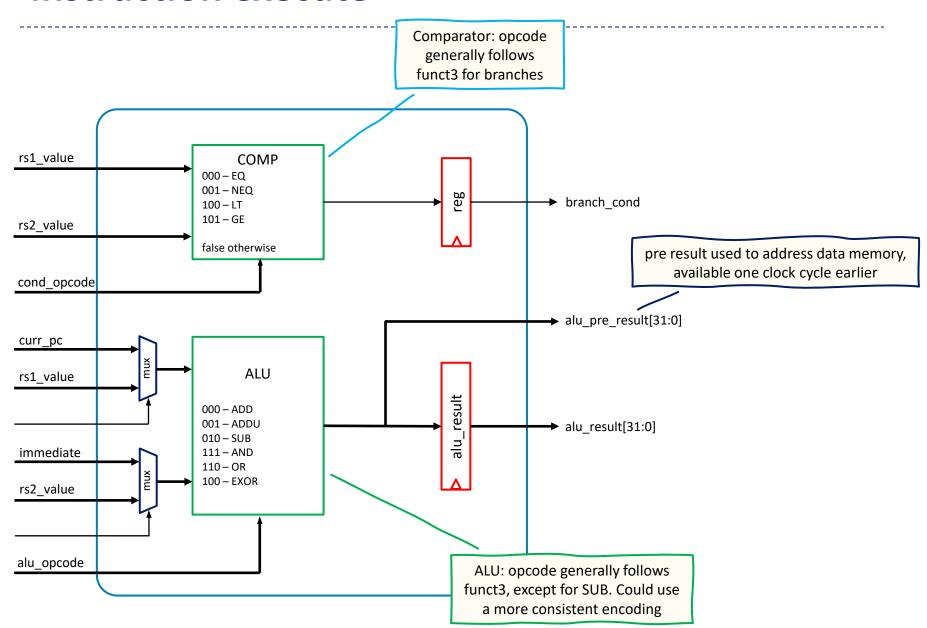

### Memory access and write back

#### Data Memory

- ▶ Implemented as 4096 words of 32 bits
  - Address is 12 bits, take only the required bits from effective address (coming from the ALU)
  - write\_en generated by control state machine
- Memory introduces one clock cycle delay
  - Take the ALU output from previous clock cycle, to get memory output during the memory phase
  - Write value (rs2) already available since end of decode phase

#### Destination register value selection


 Could be the next\_pc (for JAL), the ALU result (for ALU operations), or the memory output (for loads)

#### Value of program counter

- Next instruction at next\_pc (for ALU operations, loads, stores, and not taken branches)
- Next instruction at alu\_result (for Jumps and taken branches)
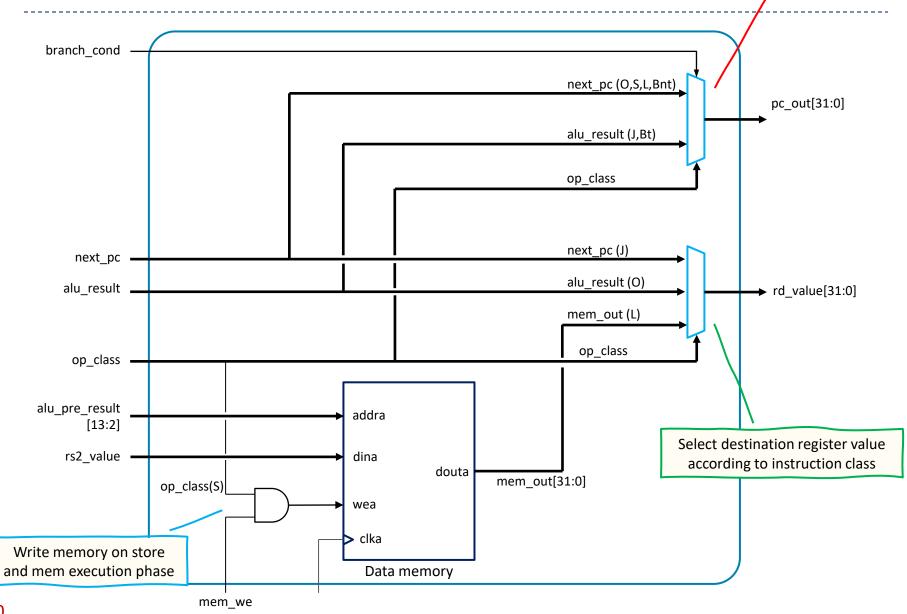
## Memory and write back

Select next pc according to instruction class and branch condition



#### **Control state machine**

### Schedules certain write operations

- Updating the program counter
- Writing into the register file
- Writing into memory
- Uses op\_class to decide
  - Plus keeps track of the phase of execution

### **Phases**

